

Exp. No. :


Date :

**FEED BACK AMPLIFIER (CURRENT SERIES)**

**AIM:** To determine the following Bandwidth, Input & Output impedances, voltage gain, current gain and power gain of the Voltage Series Feedback Amplifier.



**APPARATUS :**

S.No.	Name of the Apparatus	Range	Quantity
1.	CL100	-	2No.
2.	Power Supply	0-30V	1No.
3.	Resistors ( $\Omega$ )	22K, 12K 8.2K & 1.2K, 1.5K	Each 1No.
4.	Capacitor	10 $\mu$ F & 4.7 $\mu$ F	Each 1No.
5.	CRO	-	1No.

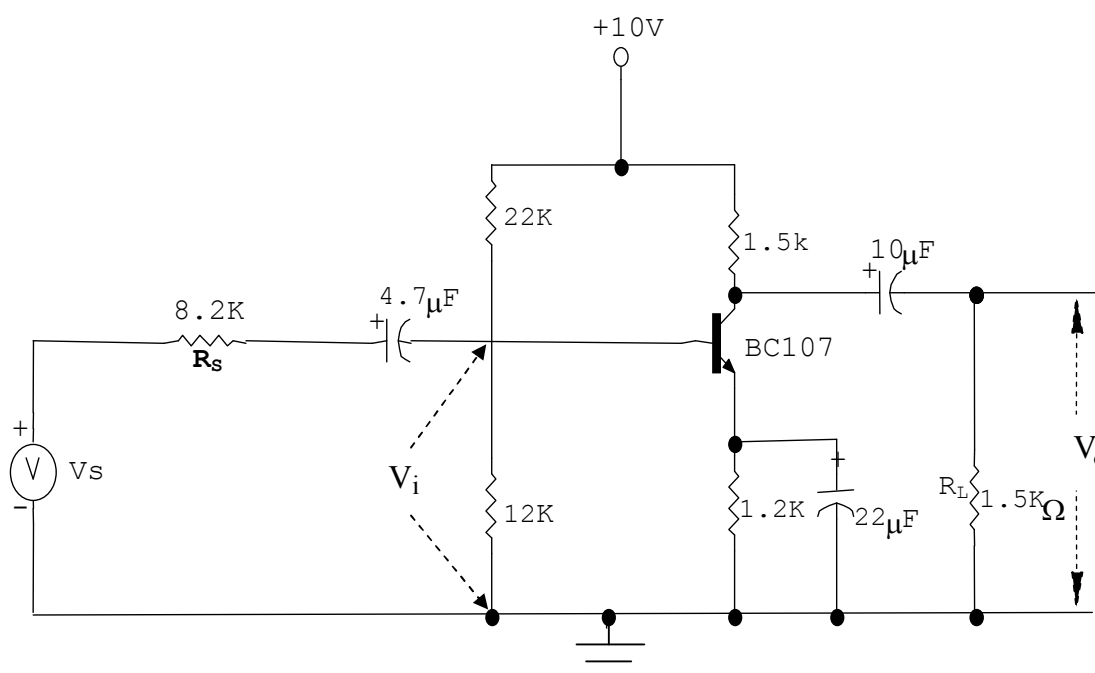**CIRCUIT DIAGRAM:**

Exp. No. :

Date :

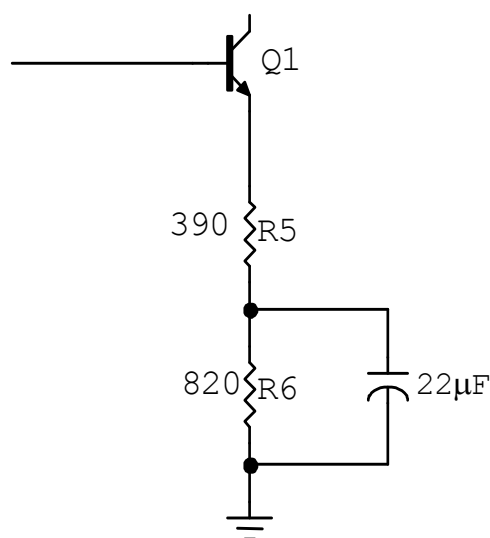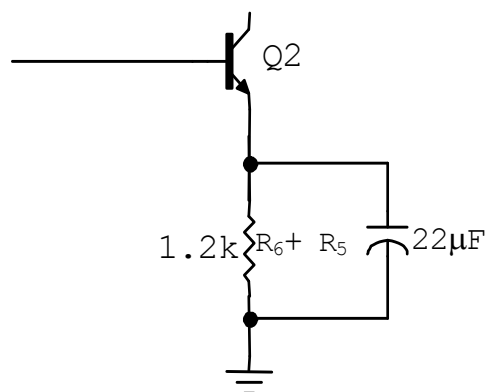**Connection for With feedback****Connection for Without feedback****PROCEDURE:**

1. Connect the circuit as shown in figure without feedback network.
2. Apply the biasing voltage of 7V.
3. Adjust the Signal generator voltage so as to get  $V_i = 15\text{mV}$  and measure  $V_s$ .
4. Vary the frequency of the signal generator from 100Hz to 1MHz, in steps and note down corresponding output voltage.
5. In the mid band range remove  $R_L$  and note down the output which is  $V_{NL}$ .
6. Connect the circuit as shown in figure with feedback network
7. Repeat the steps 2 to 5
8. Plot the frequency response and determine the bandwidth.
9. Calculate the input and output impedance in the mid band region using

**WITH FEEDBACK**

$$R_i = \frac{V_i R_s}{V_s - V_i} =$$

$$R_o = \frac{V_{NL} - V_{FL}}{V_{FL}} \times R_L =$$

**WITHOUT FEEDBACK**

$$R_i = \frac{V_i R_s}{V_s - V_i} =$$

$$R_o = \frac{V_{NL} - V_{FL}}{V_{FL}} \times R_L =$$

Date :

### WITHOUT FEEDBACK

$$A_I = \frac{I_o}{I_i} =$$

$$I_O = \frac{V_O}{R_O} =$$

$$A_V = \frac{V_o}{V_i} =$$

$$I_i = \frac{V_s - V_i}{R_s} =$$


**Power gain( $A_p$ )=  $A_v \cdot A_i$  =**

[illegible]

Exp. No. :

Date :

Frequency (Hz)	$V_i$ (mV)	$V_o$ (V)	$A_v = \frac{V_o}{V_i}$	$20 \log A_v$	$V_i$ (mV)	$V_o$ (V)	$A_v = \frac{V_o}{V_i}$	$20 \log A_v$

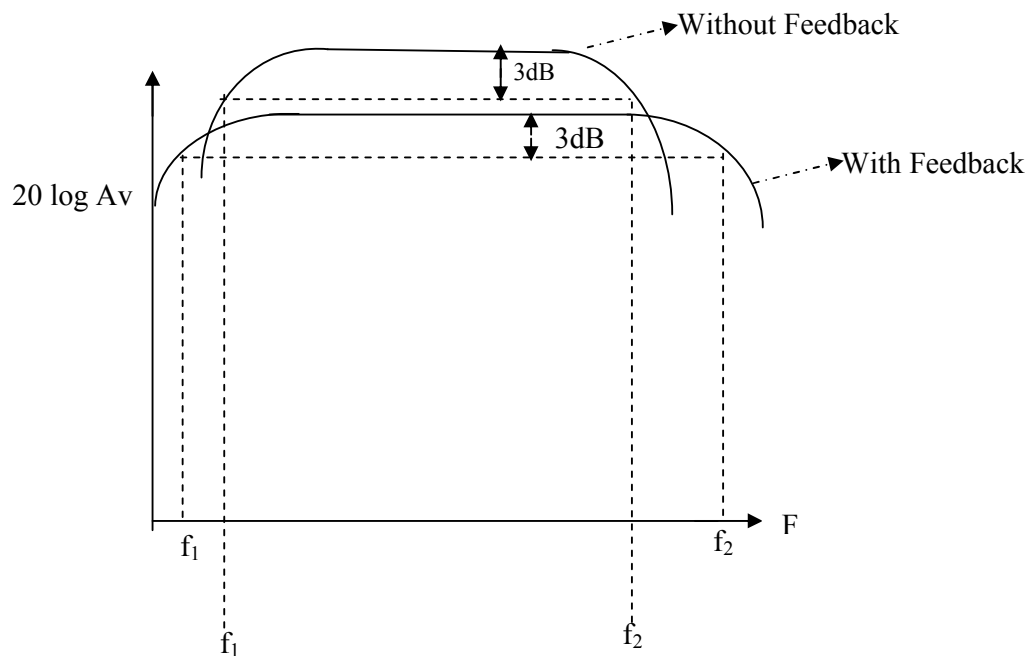**MODEL GRAPH:****Bandwidth(Without Feedback)**

$$f_2 - f_1 =$$

**Bandwidth(Without Feedback)**

$$f_2 - f_1 =$$

Exp. No. :

Date :

**RESULTS:****WITH FEEDBACK**Input impedance( $R_i$ ) =Current gain( $A_i$ ) =Output impedance( $R_o$ ) =Voltage gain( $A_v$ ) =Power gain( $A_p$ ) =

Bandwidth =

**WITHOUT FEEDBACK**Input impedance( $R_i$ ) =Current gain( $A_i$ ) =Output impedance( $R_o$ ) =Voltage gain( $A_v$ ) =Power gain( $A_p$ ) =

Bandwidth =