

Exp. No.:

Date:


FEEDBACK AMPLIFIER (VOLTAGE SERIES)

AIM: To determine Bandwidth, Input & Output impedances, voltage gain, current gain and power gain of the Voltage Series Feedback Amplifier.

APPARATUS :

S.No.	Name of the Apparatus	Range	Quantity
1.	CL100	-	2No.
2.	Power Supply	0-30V	1No.
3.	Resistors (Ω)	100K, 10K, 4.7K	Each 2No.
		4.7K, 1K, 1.5K, 100	Each 1No.
4.	Capacitor	4.7 μ F,	3No.
		10 μ F	
5.	CRO	-	1No.

CIRCUIT DIAGRAM:

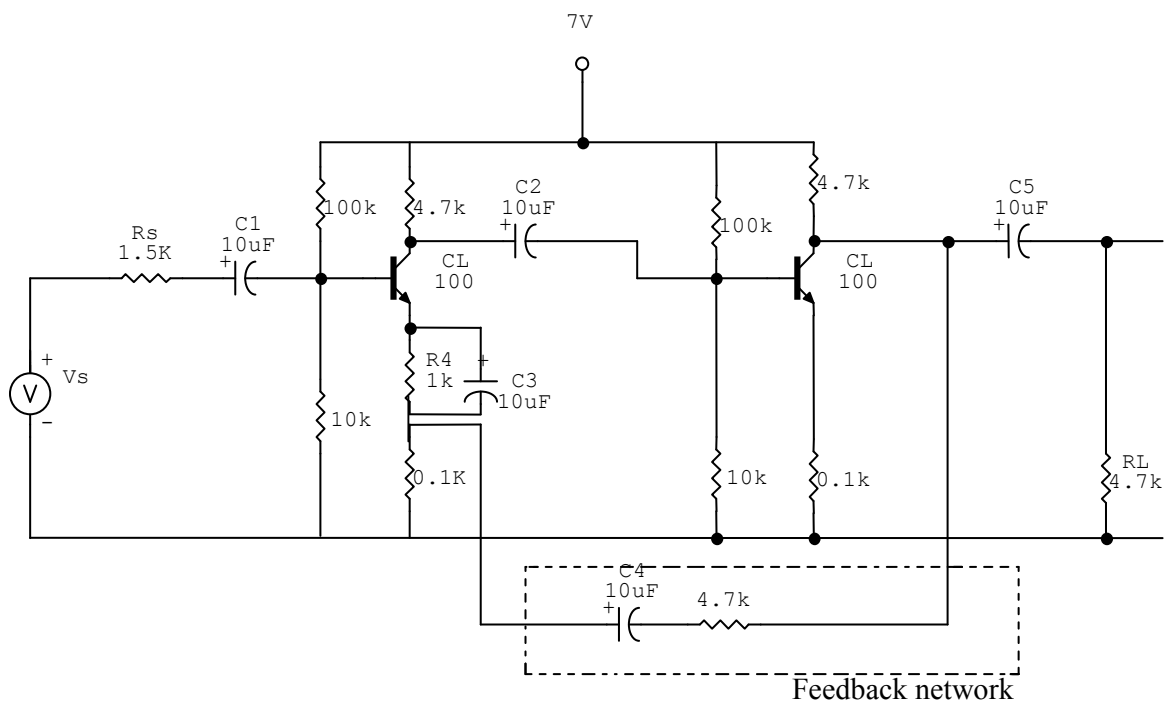

PROCEDURE:

1. Connect the circuit as shown in figure without feedback network.
2. Apply the biasing voltage of 7V.

Exp. No.:

Date:

3. Adjust the Signal generator voltage so as to get $V_i = 15\text{mV}$ and measure V_s .
4. Vary the frequency of the signal generator from 100Hz to 1MHz, in steps and note down corresponding output voltage.
5. In the mid band range remove R_L and note down the output which is V_{NL} .
6. Connect the circuit as shown in figure with feedback network
7. Repeat the steps 2 to 5
8. Plot the frequency response and determine the bandwidth.
9. Calculate the input and output impedance in the mid band region using

WITH FEEDBACK

$$R_i = \frac{V_i R_s}{V_s - V_i} =$$

$$R_o = \frac{V_{NL} - V_{FL}}{V_{FL}} \times R_L =$$

WITHOUT FEEDBACK

$$R_i = \frac{V_i R_s}{V_s - V_i} =$$

$$R_o = \frac{V_{NL} - V_{FL}}{V_{FL}} \times R_L =$$

8. Calculate the current gain A_i , voltage gain A_v and power gain (A_p) using

WITH FEEDBACK

$$A_i = \frac{I_o}{I_i} =$$

$$I_o = \frac{V_o}{R_o} =$$

$$A_v = \frac{V_o}{V_i} =$$

$$I_i = \frac{V_s - V_i}{R_s} =$$

WITHOUT FEEDBACK

$$A_i = \frac{I_o}{I_i} =$$

$$I_o = \frac{V_o}{R_o} =$$

$$A_v = \frac{V_o}{V_i} =$$

$$I_i = \frac{V_s - V_i}{R_s} =$$


Date:

Power gain(A_P)= $A_V \cdot A_I$ =

[illegible]

Exp. No.:

Date:

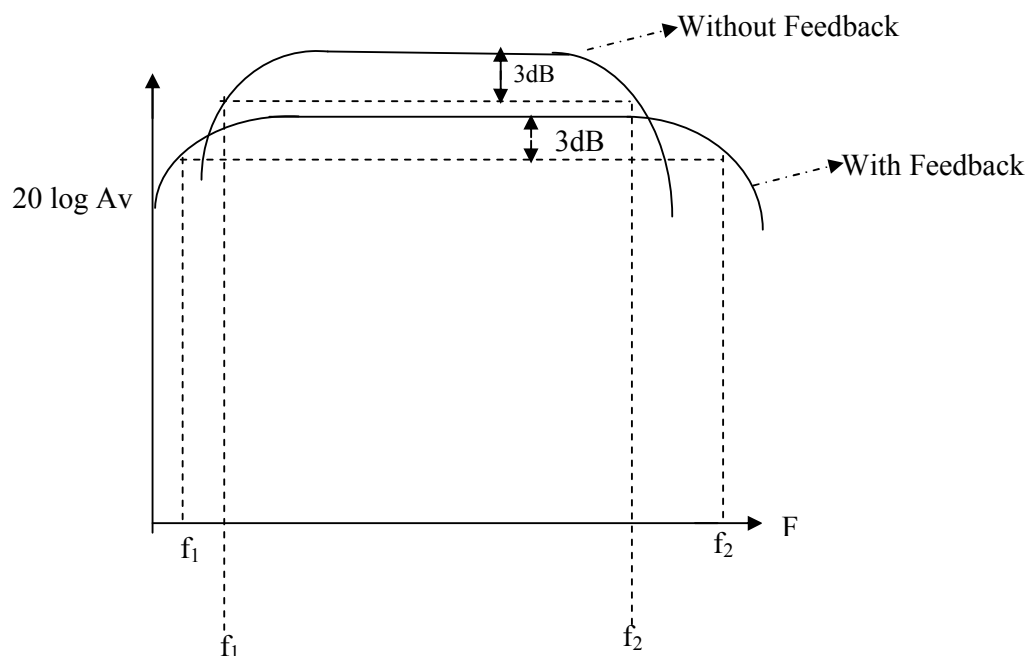MODEL GRAPH:**Bandwidth**(Without Feedback)

$$f_2 - f_1 =$$

Bandwidth(Without Feedback)

$$f_2 - f_1 =$$

RESULTS:**WITH FEEDBACK**Input impedance(R_i) =Current gain(A_i) =Output impedance(R_o) =Voltage gain(A_v) =Power gain(A_p) =

Bandwidth =

WITHOUT FEEDBACKInput impedance(R_i) =Current gain(A_i) =Output impedance(R_o) =Voltage gain(A_v) =Power gain(A_p) =

Bandwidth =