

Exp.No.:

Date :


## TRANSISTOR CB CHARACTERISTICS (INPUT & OUTPUT)

**AIM :** To obtain the input and output characteristics of a Transistor in CB configuration and also determine the hybrid parameters.

### APPARATUS :

S.No.	Name of the Apparatus	Range	Quantity
1.	BC107	-	1No.
2.	Power Supply	0-30V	2No.
3.	Ammeter	0-10mA	2No.
4.	Voltmeter	0-5V, 0-10V	Each 1No.
5.	Resistor	1.2K $\Omega$	1No.

### CIRCUIT DIAGRAM:

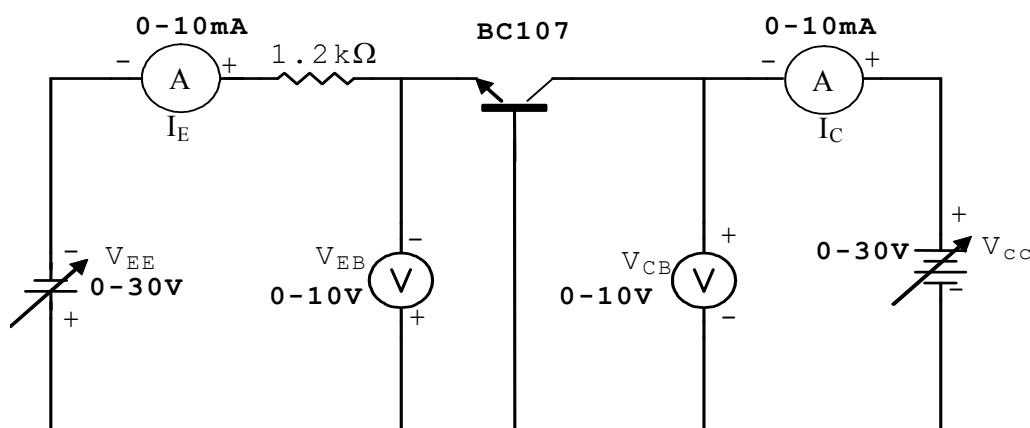

### PROCEDURE:

1. Connect the circuit as shown in figure.
2. For output characteristics Keep  $I_E = 2\text{mA}$  by varying  $V_{EE}$ .
3. Vary  $V_{CC}$  in steps and note down  $I_C$  and  $V_{CB}$ .
4. Repeat step 3 for  $I_E = 4\text{mA}$  and  $6\text{mA}$ .
5. Draw the output characteristics by taking  $V_{CB}$  on X-axis and  $I_C$  on Y-axis for different values of  $I_E$ .
6. For input characteristics Keep  $V_{CB} = 0$ , Vary  $V_{EE}$  in steps and note down  $I_E$  and  $V_{EB}$ .
8. Repeat step 6 for  $V_{CB} = 1\text{V}$  and  $V_{CB} = 2\text{V}$

Exp.No.:

Date :


9. Draw the input characteristics by taking  $V_{EB}$  on X-axis and  $I_E$  on Y-axis for different values of  $V_{CB}$ .

**READINGS :****a: Output Characteristics**

$I_E = 2\text{mA}$		$I_E = 4\text{mA}$		$I_E = 6\text{mA}$	
$V_{CB}$ (V)	$I_C$ (mA)	$V_{CB}$ (V)	$I_C$ (mA)	$V_{CB}$ (V)	$I_C$ (mA)

**b: Input Characteristics**

$V_{CB} = 0\text{V}$		$V_{CB} = 1\text{V}$		$V_{CB} = 2\text{V}$	
$V_{EB}$ (V)	$I_E$ (mA)	$V_{EB}$ (V)	$I_E$ (mA)	$V_{EB}$ (V)	$I_E$ (mA)

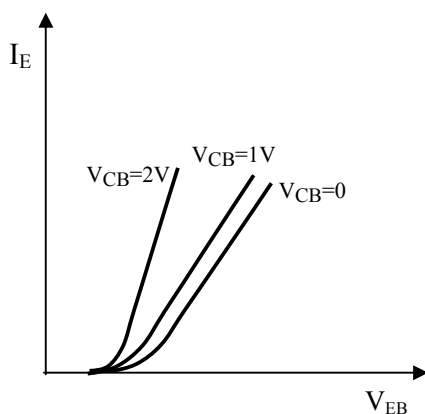
**MODEL GRAPHS:****Input Characteristics**

$$h_{ib} = \left. \frac{\Delta V_{EB}}{\Delta I_E} \right|_{V_{CB} \text{ constant}} =$$

$$h_{rb} = \left. \frac{\Delta V_{EB}}{\Delta V_{CB}} \right|_{I_E \text{ constant}} =$$

Exp.No.:

Date :

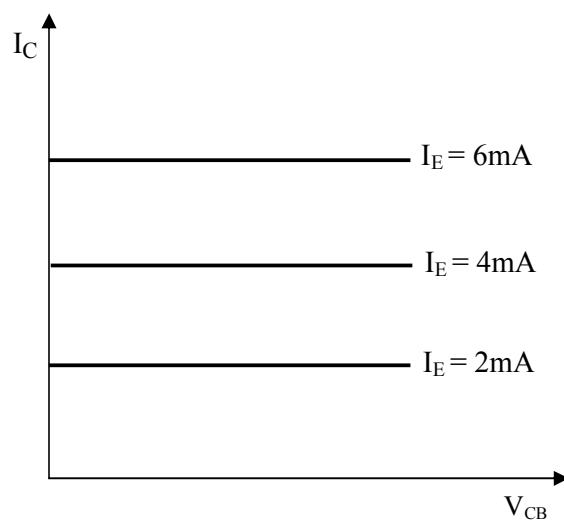**Output Characteristics:**

$$h_{fb} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} \text{ cons } \tan t} =$$

$$h_{ob} = \left. \frac{\Delta I_C}{\Delta V_{CB}} \right|_{I_E \text{ cons } \tan t} =$$

**RESULTS:**

1. Input Impedance,  $h_{ib} =$
2. Output admittance,  $h_{ob} =$
3. Forward current gain,  $h_{fb} =$
4. Reverse voltage gain,  $h_{rb} =$