

Exp. No.:

Date:


## CC AMPLIFIER (EMITTER FOLLOWER)

**AIM:** To determine Bandwidth, Input & Output impedances, voltage gain, current gain and Power gain of the CE Amplifier

### APPARATUS :

| S.No. | Name of the Apparatus  | Range                       | Quantity  |
|-------|------------------------|-----------------------------|-----------|
| 1.    | BC107                  | -                           | 1No.      |
| 2.    | Power Supply           | 0-30V                       | 1No.      |
| 3.    | Resistors ( $\Omega$ ) | 100K, 39K, 27K, 2.2K & 1.5K | Each 1No. |
| 4.    | Capacitor              | 1 $\mu$ F                   | 1No.      |
| 5.    | CRO                    | -                           | 1No.      |

### CIRCUIT DIAGRAM:

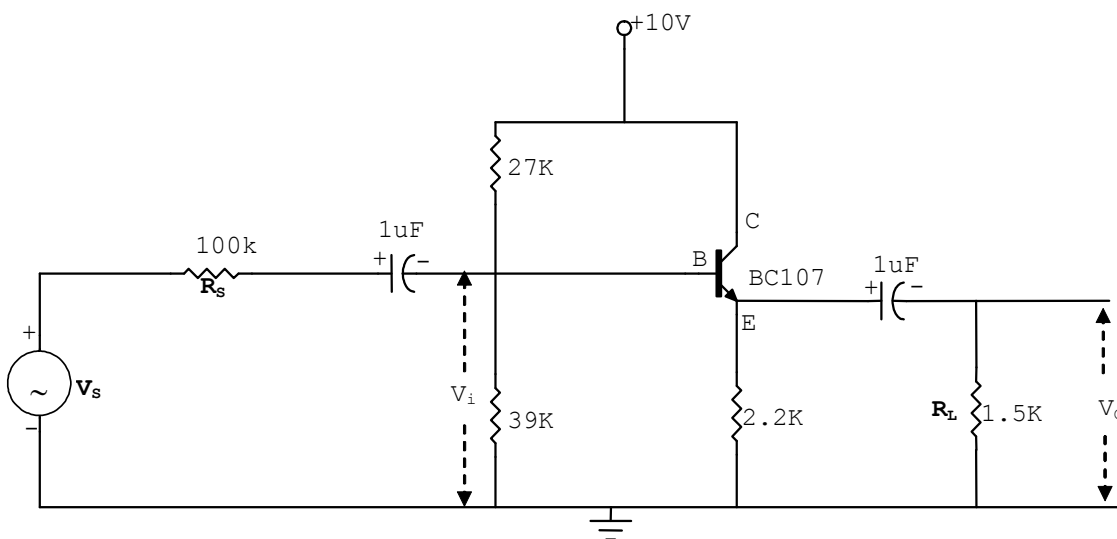

### PROCEDURE:


1. Connect the circuit as shown in figure.
2. Apply the biasing voltage of 10 V.
3. Adjust the Signal generator voltage so as to get  $V_i = 1V$  and measure  $V_s$ .
4. Vary the frequency of the signal generator from 100Hz to 1MHz, in steps and note down corresponding output voltage.
5. In the mid band range remove  $R_L$  and note down the output which is  $V_{NL}$ .

Date:

Exp. No.:

Date:

| S No. | Frequency (Hz) | $V_i$ (V) | $V_o$ (V) | $A_v = \frac{V_o}{V_i}$ | $20 \log A_v$ |
|-------|----------------|-----------|-----------|-------------------------|---------------|
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |
|       |                |           |           |                         |               |

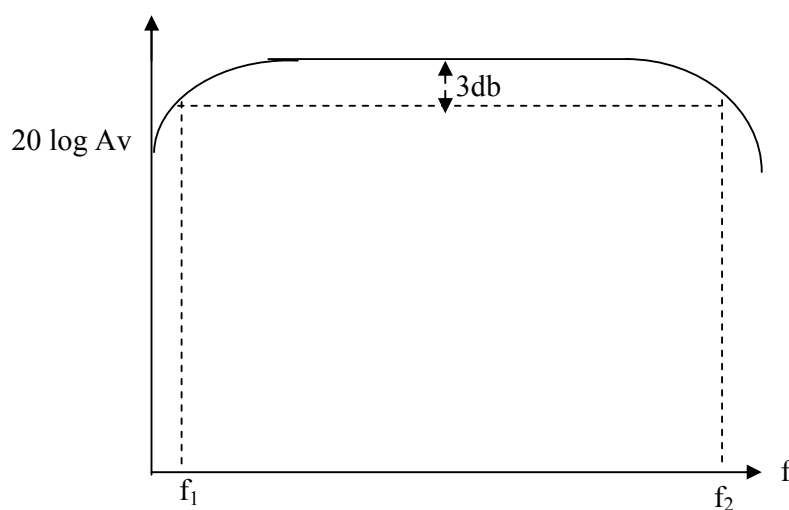**MODEL GRAPH:**

$$\text{Bandwidth} = f_2 - f_1 =$$

**RESULTS:** Input impedance( $R_i$ ) =Output impedance( $R_o$ ) =Current gain( $A_i$ ) =Voltage gain( $A_v$ ) =Power gain( $A_p$ ) =

Bandwidth =