

Exp. No.:

Date:


### RC PHASE-SHIFT OSCILLATOR

**AIM :** To determine the frequency of the RC phase-shift oscillator and also determine the Phase difference at each RC Network.

**APPARATUS :**

S.No.	Name of the Apparatus	Range	Quantity
1.	SL100	-	1No.
2.	Power Supply	0-30V	1No.
3.	Resistors ( $\Omega$ )	560K, 22K, 8.2K, 5.6K, 3.9K & 3.9K	Each 1No.
4.	Capacitor	22 $\mu$ F,	1No.
		0.01 $\mu$ F	3No.
5.	CRO	-	1No.

**CIRCUIT DIAGRAM:**

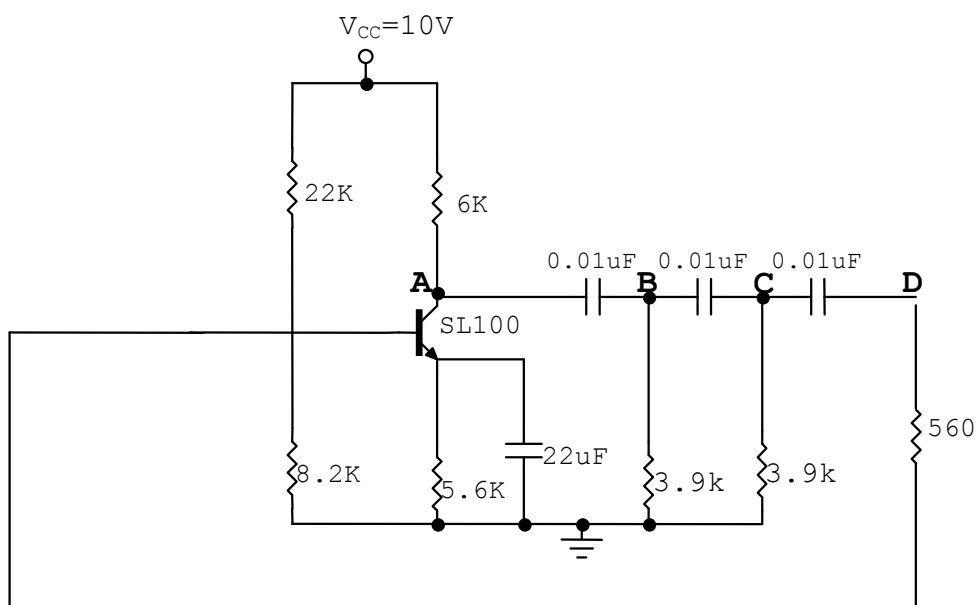

**PROCEDURE:**

1. Connect the circuit as shown in figure.
2. Set  $V_{CC} = 10V$ .
3. Observe the output waveform at Point **A** on CRO and measure the frequency.

Exp. No.:

Date:

4. Calculate the phase difference between the points **A&B, A&C and A&D** using

$$\theta = \frac{d}{D} \times 360^\circ$$

Where d is the distance between adjacent peaks.

D is the time period of the output waveform.

Theoretical frequency is calculated using


$$f = \frac{1}{2\pi RC\sqrt{6+4K}} \text{ Hz}$$

$$\text{Where } K = \frac{R_c}{R} =$$

$$R = R_1 = R_2 = 3.9 \text{ K}$$

=

#### MODEL WAVEFORM :

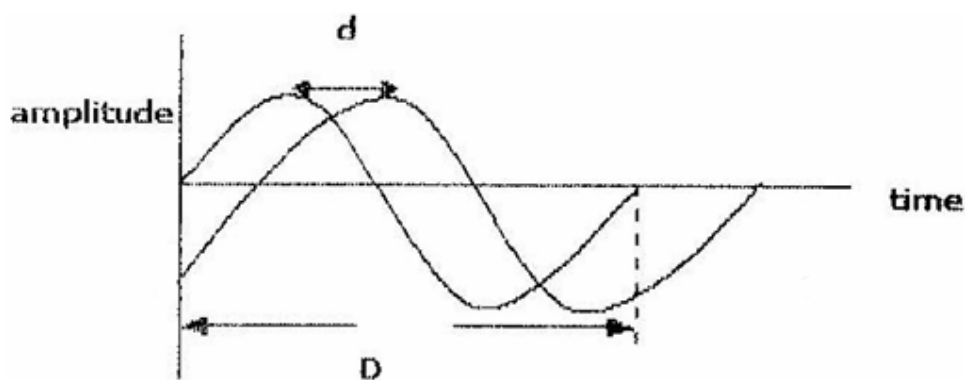

#### TABULATION:

Between	d	D	Phase Difference $\theta = \frac{d}{D} \times 360^\circ$
<b>A&amp;B</b>			
<b>A&amp;C</b>			
<b>A&amp;D</b>			

#### RESULTS:

Practical frequency =

Theoretical frequency =