

Exp. No.

Date :

ZENER DIODE CHARACTERISTICS

AIM : a) To determine zener breakdown voltage and zener resistance from reverse characteristic.

b) To determine zener voltage regulation characteristics.

APPARATUS :

S.No.	Name of the Apparatus	Range	Quantity
1.	BZX 6.2	-	1No.
2.	Power Supply	0-30V	1No.
3.	Ammeter	0-50mA	1No.
4.	Voltmeter	0-5V	1No.
5.	Resistor	390 Ω	1No.

CIRCUIT DIAGRAM :

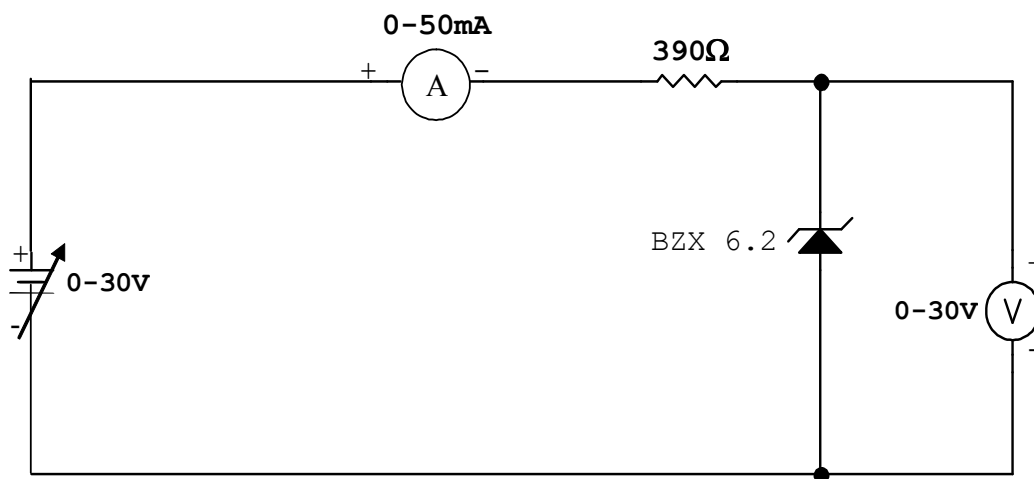
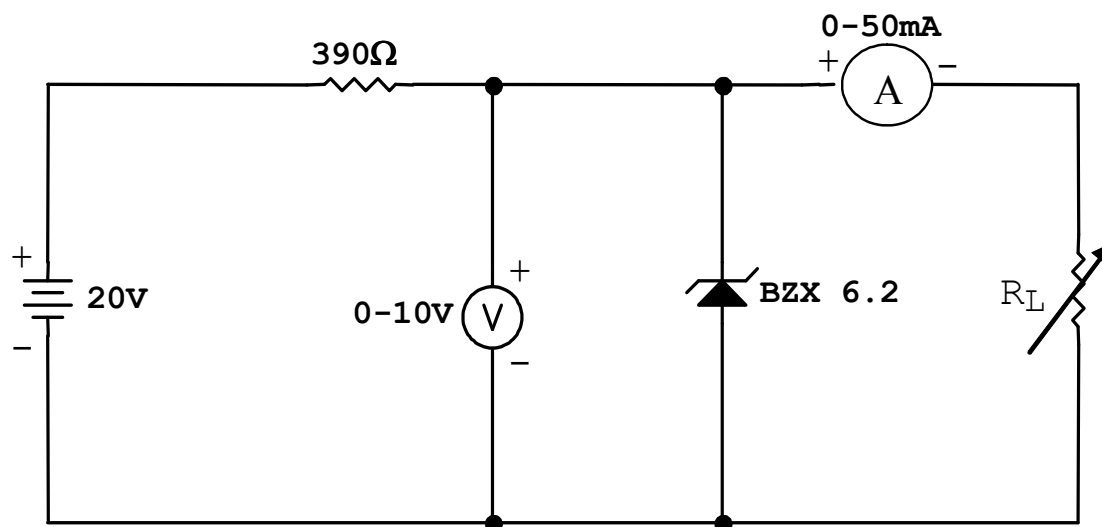


Fig 1: V-I Characteristics

Exp. No.

Date :

**Fig-2: Voltage Regulation****PROCEDURE:**

1. Connect the circuit as shown in fig.1 for V-I characteristics.
2. Vary the supply voltage in steps and note down the voltage across the zener and current flowing through it.
3. Connect the circuit as shown in fig. 2 for voltage regulation characteristics.
4. Fix the supply voltage at 20V.
5. Change the load resistance R_L and note down V_Z and I_L (up to 30mA).
6. Plot V-I and Voltage Regulation characteristics.
7. From the graph
 - a) find Zener breakdown voltage (at which current increases rapidly).

b) find the Zener resistance using $R_Z = \frac{V}{I}$

c) calculate % regulation = $\frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$

Exp. No.

Date :



READINGS:**a. V-I Characteristic**

S.No.	V _z (V)	I _z (mA)

b. Voltage regulation Characteristic

SNo.	I _L (mA)	V _z (V)

$$\% \text{ regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 =$$

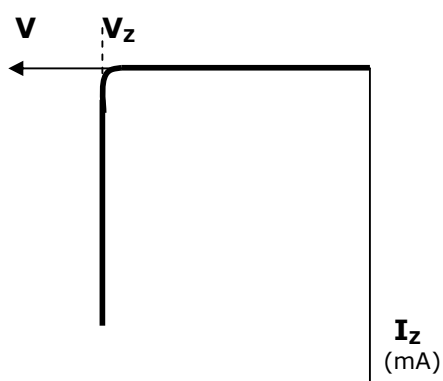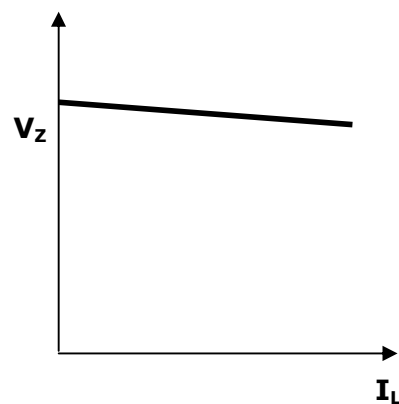MODEL GRAPHS:**V-I Characteristic****Voltage regulation characteristic****RESULTS:**

1. Zener breakdown voltage =
2. Zener resistance =
3. % regulation =